[Download](#)[Favorite](#)[Classes \(/classes/\)](#)[Contests \(/contest/\)](#)[Community \(/topics/\)](#)[Teachers \(/teachers/\)](#)[Autodesk \(/advertisements/\)](http://www.autodesk.com)

advertisement

DIY MUSCLE SENSOR / EMG CIRCUIT FOR A MICROCONTROLLER

By Advancer Technologies (/member/Advancer+Technologies/) in Technology (/technology/) > Science (/technology

[/science/\)](#)


608,213

765

426

Featured

Published Jun. 27, 2011

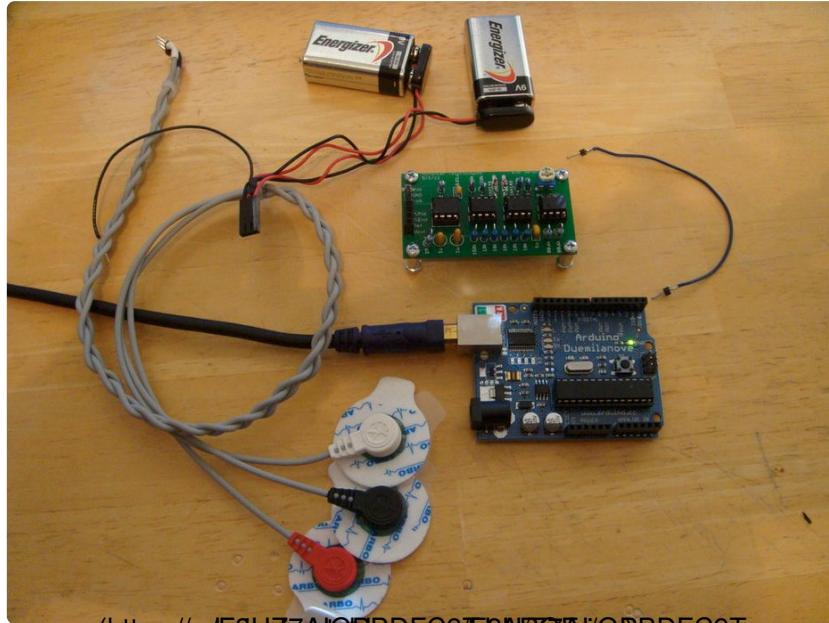[Download](#)[Favorite](#)[\(/member](#)[/Advancer%20Technologies/\)](#)By **Advancer
Technologies**

1 of 29

7/16/18, 12:34 PM

DIY Member

/EMG Sensor / EMG Circuit for a Microcontr...

<http://www.instructables.com/id/Muscle-EMG-Sen...>

DIY Muscle Sensor / EMG Circuit for a Microcontroller by Advancer Technologies (/member/Advancer Technolog

/Advancer%20Technologies/)

Advancer Technologies

(<http://www.advancertechnologies.com>)

Follow

More by

the author:



About: The bionics wizards at Advancer Technologies are changing the world by helping homegrown inventors flex their creative muscles. From robots to video games to prosthetics, their muscle sensor, MyoWare®,... More About

Advancer Technologies » (/member/Advancer%20Technologies/)

Download

Favorite

Measuring muscle activation via electric potential, referred to as electromyography (EMG) (<http://en.wikipedia.org/wiki/Electromyography>), has traditionally been used for medical research and diagnosis of neuromuscular disorders. However, with the advent of ever shrinking yet more powerful microcontrollers and integrated circuits, EMG circuits and sensors have found their way into prosthetics, robotics and other control systems. Yet, EMG systems remain expensive and mostly outside the grasp of modern hobbyist.

advertisement

This instructable will teach you how to make your own muscle sensor / EMG circuit to incorporate into your next project. Use it to control video games, robot arms, exoskeletons, etc.

on how to hook up and use your EMG circuit

board!

Download

Favorite

Muscle Sensor / EMG Circuit Demo



You can now also purchase EMG sensors, kits, cables and electrodes at

www.AdvancerTechnologies.com

[\(\[http://www.advancertechnologies.com/p/shop_3.html\]\(http://www.advancertechnologies.com/p/shop_3.html\)\)!](http://www.advancertechnologies.com/p/shop_3.html)

[Muscle Sensor Kit](http://www.advancertechnologies.com/p/muscle-sensor-v3.html)

[\(<http://www.advancertechnologies.com/p/muscle-sensor-v3.html>\) \(now also on SparkFun \(<https://www.sparkfun.com/products/11776>\)\)](http://www.advancertechnologies.com/p/muscle-sensor-v3.html)

[Muscle Sensor Electrodes](http://www.advancertechnologies.com/p/muscle-sensor-electrodes.html)

[\(<http://www.advancertechnologies.com/p/muscle-sensor-electrodes.html>\)](http://www.advancertechnologies.com/p/muscle-sensor-electrodes.html)

Note: This sensor is not intended for use in the

advertisements

diagnosis of disease or other conditions, or in
the cure, mitigation treatment, or prevention of
disease, in a man or other animals.

[Download](#)

[Favorite](#)

About Advancer Technologies

Advancer Technologies

(<http://www.advancertechnologies.com/>) is a company devoted to developing innovative game-changing biomedical and biomechanical technologies and applied sciences.

Additionally, Advancer Technologies

(<http://www.advancertechnologies.com/>) promotes all forms of interest and learning into biomedical technologies. To help culture and educate future great minds and concepts in the field, they frequently post informative instructions on some of their technologies. For more information, please visit

www.AdvancerTechnologies.com

(<http://www.advancertechnologies.com/>) .


 Add Tip

 Ask Question

 Comment

[Download](#)

Step 1: Materials

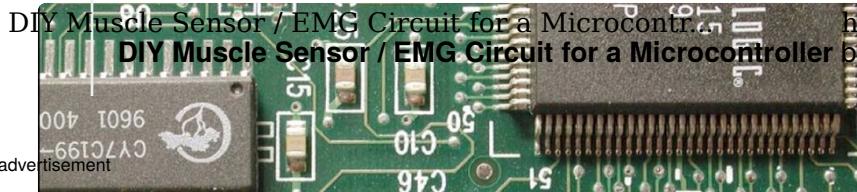

Download

Favorite

Materials

Click on the links to go to where you can buy items/order free samples.

Circuit Chips

3x [TL072 IC Chip](http://focus.ti.com/docs/prod/folders/print/tl072.html) (<http://focus.ti.com/docs/prod/folders/print/tl072.html>) - Free Samples

1x [INA106 IC Chip](http://focus.ti.com/docs/prod/folders/print/ina106.html) (<http://focus.ti.com/docs/prod/folders/print/ina106.html>) - Free Samples

Cables and Electrodes

1x [EMG Cables](http://bio-medical.com/products/din-ekgemgeeg-snap-leads-24-inch.html) (<http://bio-medical.com/products/din-ekgemgeeg-snap-leads-24-inch.html>) (set of 3)... Note: you could optionally connect the alligator clips directly to the electrodes.

3x [EMG Electrodes](http://bio-medical.com/products/kendall-tyco-arbo-disposable-electrodes-50pkg-35mm.html) (<http://bio-medical.com/products/kendall-tyco-arbo-disposable-electrodes-50pkg-35mm.html>)

Power

5 of 39

2x 9V Battery

7/16/18, 12:34 PM

Capacitors

- 2x 1.0 uF Tant (http://search.digikey.com/scripts/DkSearch/dksus.dll?WT.z_header=search_go&lang=en&site=us&keywords=399-3529-ND&x=0&y=0)
- 1x 0.01 uF Ceramic Disc (http://search.digikey.com/scripts/DkSearch/dksus.dll?WT.z_header=search_go&lang=en&site=us&keywords=490-3812-ND&x=0&y=0)
- 1x 1.0 uF Ceramic Disc (http://search.digikey.com/scripts/DkSearch/dksus.dll?WT.z_header=search_go&lang=en&site=us&keywords=399-4389-ND&x=0&y=0)

Resistors

- 3x 150 kOhm 1% (<http://search.digikey.com/scripts/DkSearch/dksus.dll?Detail&name=150KXBK-ND>)
- 2x 1 MOhm 1% (<http://search.digikey.com/scripts/DkSearch/dksus.dll?Detail&name=RNF14FTD1M00CT-ND>)
- 2x 80.6 kOhm 1% (<http://search.digikey.com/scripts/DkSearch/dksus.dll?Detail&name=RNF14FTD80K6CT-ND>) (Note: You don't need exactly 80.6k resistors. Anything around 80k should suffice.)

- 6x 10 kOhm 1% (<http://search.digikey.com>

advertisement
[Download](#)[Favorite](#)[/scripts/DkSearch](#)[/dksus.dll?Detail&name=10.0KXBK-ND\)](#)

- 1x 100 kOhm Trimmer

[\(http://search.digikey.com/scripts/DkSearch](#)[/dksus.dll?WT.z_header=search_go&lang=en&site=us&keywords=D4AA15-ND&x=0&y=0\)](#)

- 1x 1 kOhm 1% (<http://search.digikey.com>

[/scripts/DkSearch](#)[/dksus.dll?Detail&name=RNF14FTD1K00CT-](#)[ND\)](#)

Misc

- 2x 1N4148 Diode (<http://search.digikey.com>

[/scripts/DkSearch](#)[/dksus.dll?WT.z_header=search_go&lang=en&site=us&keywords=1N4148FS-ND&x=0&y=0\)](#)

- Jumper wires (<http://www.radioshack.com>

[/product/index.jsp?productId=2103801\)](#)

- 3x Alligator clip cables

[\(http://www.sparkfun.com/products/8927\)](#)

Optional

- 1x Oscilloscope


- 1x Multimeter

[!\[\]\(f8f63333e9701d869b3a17c610b5636e_img.jpg\) Add Tip](#)[!\[\]\(9033280e3e1a3e4096a67f3c99a0cdee_img.jpg\) Ask Question](#)[!\[\]\(481b3a1bc27da3029f4c9642b320d18b_img.jpg\) Comment](#)[Download](#)

Download

Favorite

advertisement

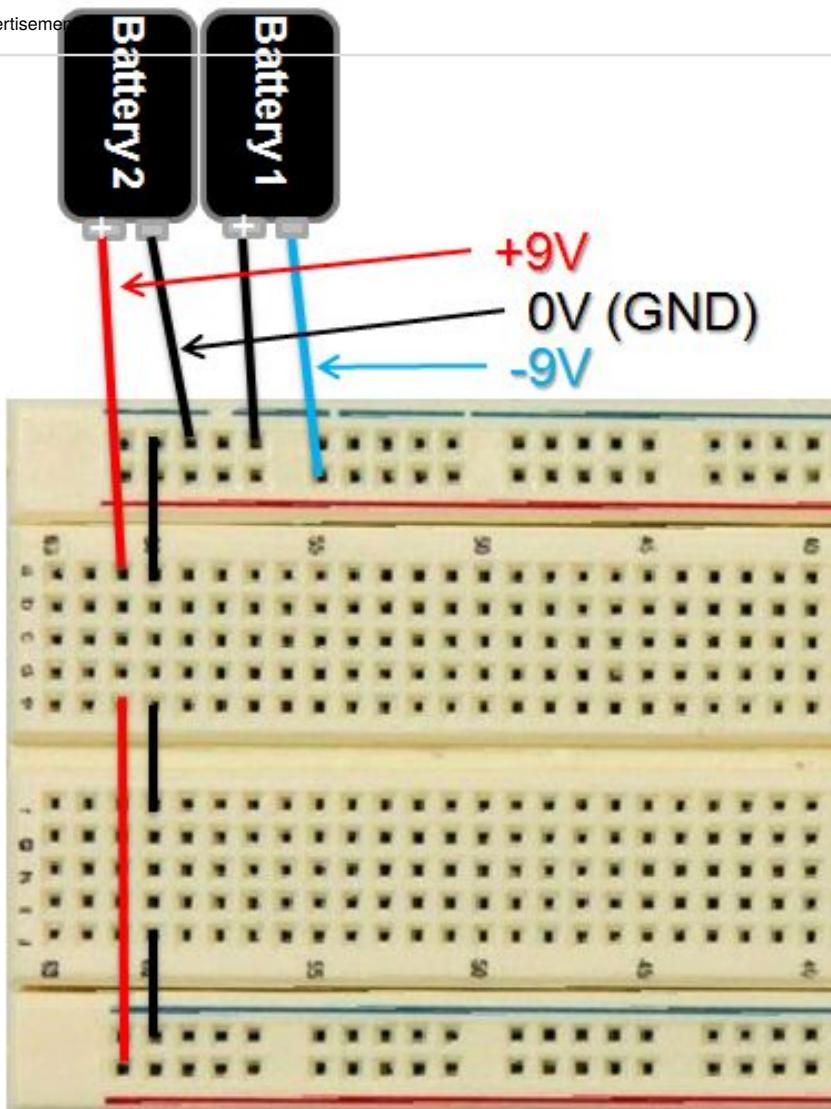

To start things off, you'll need both a positive and negative voltage power supply. We will make these using two 9V batteries.

Now, everyone knows what a positive voltage power supply is, (e.g. common battery) but how do you go about making a negative 8 volt voltage power supply?

Common electrical circuit rule of thumb is

when you connect two batteries in series (eg

[Download](#)[Favorite](#)

positive terminal of battery 1 connected to the negative terminal of battery 2) then measure the voltage from the negative terminal of battery 1 and the positive terminal of battery 2, the measured voltage is equal to the summation of the voltages of battery 1 and battery 2.

For this circuit we want a +9V and a -9V power supplies. If we connect our two 9V batteries in series, we will get a power supply of +18V. So how do we get the -9V from these two?

It might help to think about what voltage actually means... voltage is an electrical potential difference. The keyword here is difference. Voltages are only meaningful in terms of the reference point (or more commonly referred to as ground). A voltage is the electrical potential between this reference point and the point you are measuring. Do you see the answer yet?

We do indeed get a +18V voltage reading if we use battery 1's negative terminal as the reference point... but what if we choose the

9 V connection between battery 1's positive

7/16/18, 12:34 PM

DIY Muscle Sensor / EMG Circuit for a Microcontroller? If we use this point as our reference or ground, then battery 2's positive terminals voltage will

be +9V and battery 1's negative terminal will be -9V!

[Download](#)

[Favorite](#)

Using your breadboard, 9V batteries and battery clips, connect the battery clip wires as shown. *However, for the time being, disconnect the positive terminal of battery 2 and the negative terminal of battery 1. It is good practice to always disconnect your power while you assemble a circuit. At the end of the assembly we will reconnect these wires to power the circuit on. (You could also add switches to do this)*


 Add Tip

 Ask Question

 Comment

[Download](#)

Step 3: SIGNAL ACQUISITION

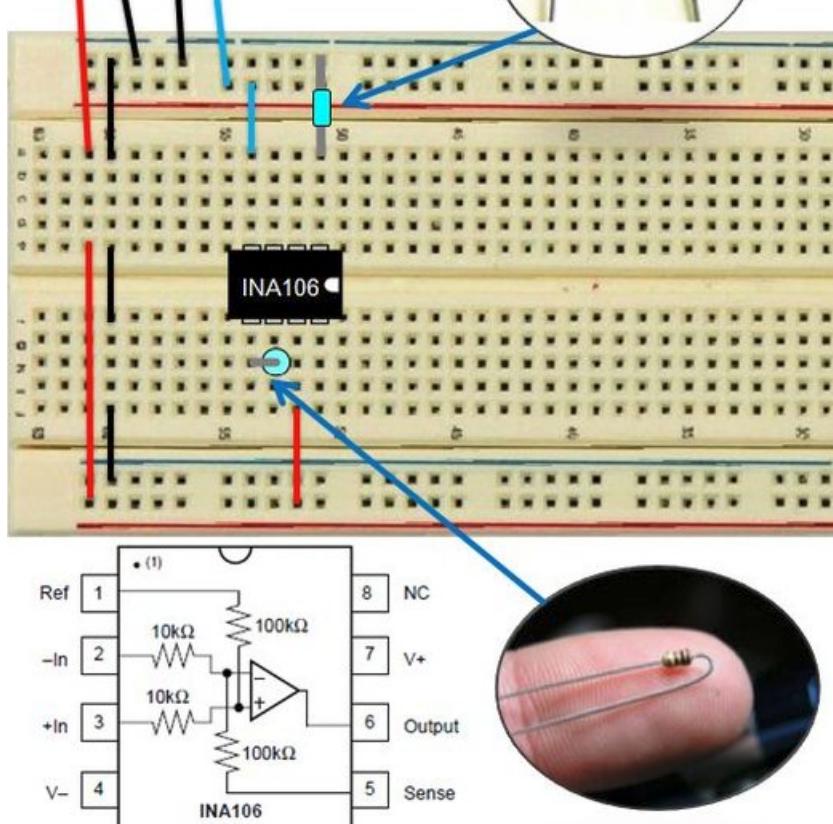[Download](#)[Favorite](#)

Next, we will work on the signal acquisition phase of your EMG circuit which we will use to measure your body's nervous system's electrical impulses used to activate muscle fibers.

First, get out your INA106 IC chip (chip A) and insert it into your breadboard as illustrated above. The INA106 is a difference amplifier which will measure and amplify ($G=110$) the very small voltage differences between the two electrodes you place on your muscle.

and then plug them in to your breadboard like

the two examples shown. One should connect

[Download](#)

[Favorite](#)

pins 5 and 6 and the other should bridge pin 1

to your ground rail of your board.

Don't worry about the other pins of the
INA106 for now; we'll come back to those later.


Add Tip

Ask Question


Comment

[Download](#)

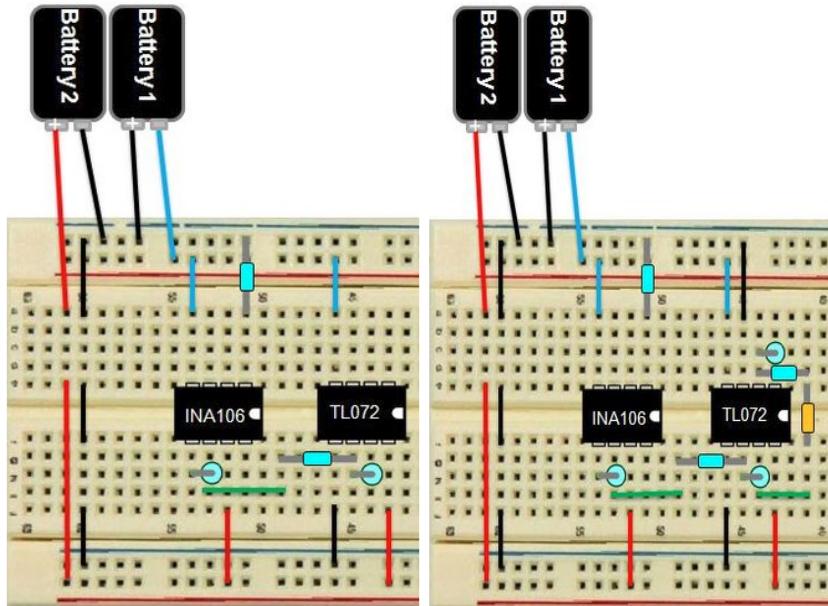
Step 4: SIGNAL CONDITIONING - Amplification



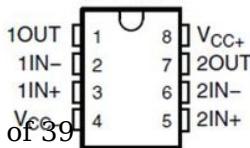TL072, TL072A, TL072B
D, JG, P, PS, OR PW PACKAGE
(TOP VIEW)



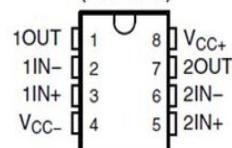TL072, TL072A, TL072B
D, JG, P, PS, OR PW PACKAGE
(TOP VIEW)



advertisment ACQUISITION phase and amplify them.

Download

Favorite

Let's start first with two series of amplification; the first will be inverting amplifier with a gain of -15. An inverting amplifier does exactly what it sounds like. It amplifies your signal but also inverts it. You can find more info about inverting amplifiers [here \(http://en.wikipedia.org/wik...\)](http://en.wikipedia.org/wiki/Operational_amplifier_applications#Inverting_amplifier).

We are going to first build an inverting amplifier with a gain of -15. To do this, we'll need one of the TL072 chips (chip B), one 150 kOhm resistor and a 10 kOhm resistor.

Place chip B as the picture indicates. Now use a jumper wire and connect pin 6 of chip A two rows past pin 8 of chip A. Grab one of the 10 kOhm resistors and plug one pin into this row as well. Connect the other pin to pin 6 of chip B. Bend a 150 kOhm resistor and connect one pin to chip B's pin 6 and the other to pin 7. You can calculate the gain by $G=-R_2/R_1$ or in this case $G=-150 \text{ kOhm} / 10 \text{ kOhm}$. (See image 1)

Next, we are going to add a capacitor to AC couple the signal. AC coupling is useful in

removing DC error offset in a signal. Read

7/16/18, 12:34 PM

Continuing on, we are going to add an active high pass filter to get rid of any DC offset and low frequency noise. To do this you will need two 150 kOhm resistors and a 0.01uF capacitor. Use a jumper wire and the 0.01 uF capacitor to bridge the center gab of your breadboard as shown. (One end of the jumper wire should be connected to pin 7 of chip B). The 150 kOhm resistor will connect the capacitor you just placed to pin 2 of chip B. Now, bend the 150 kOhm resistor and push it into connect pins 1 & 2. (See image 2)

Also, go ahead and connect chip B's pin 4 to your -9V rail, pin 8 to your +9V rail, and pins 3 & 5 to your GND rail.


 [Add Tip](#) [Ask Question](#) [Comment](#)[Download](#)

Step 5: SIGNAL CONDITIONING - Rectification

advertis



Download

Favorite

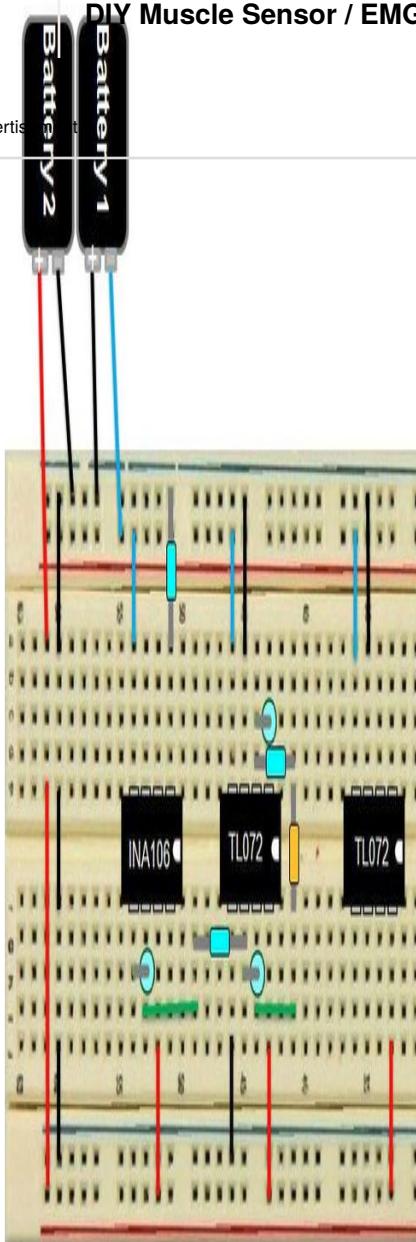



**TL072, TL072A, TL072B
D, JG, P, PS, OR PW PACKAGE
(TOP VIEW)**

1OUT	1	8	V _{CC+}
1IN-	2	7	2OUT
1IN+	3	6	2IN-
V _{CC-}	4	5	2IN+

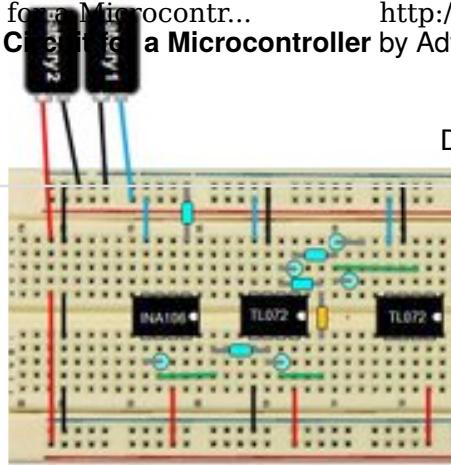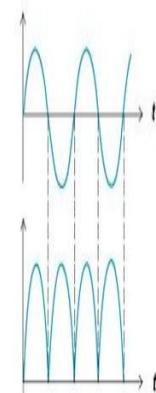

**TL072, TL072A, TL072B
D, JG, P, PS, OR PW PACKAGE
(TOP VIEW)**

1OUT	1	8	V _{CC+}
1IN-	2	7	2OUT
1IN+	3	6	2IN-
V _{CC-}	4	5	2IN+

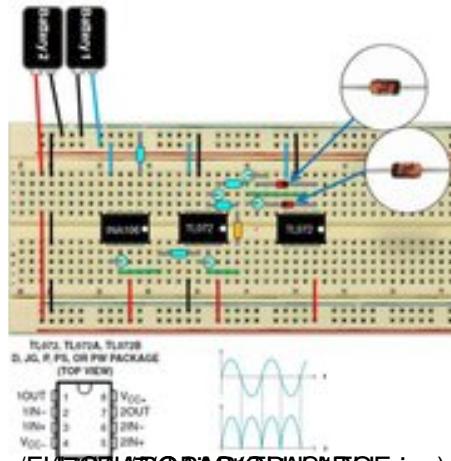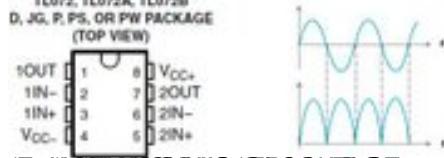

**TL072, TL072A, TL072B
D, JG, P, PS, OR PW PACKAGE
(TOP VIEW)**

1OUT	1	8	V _{CC+}
1IN-	2	7	2OUT
1IN+	3	6	2IN-
V _{CC-}	4	5	2IN+



In this phase, we will be rectifying the signal using an active full-wave rectifier (<http://en.wikipedia.org/wiki/Rectifier#Full->

negative portion of our signal and turn it

advertisement

positive so the entire signal falls within the positive voltage region. We will use this coupled with a low pass filter to turn our AC signal in to a DC voltage; readying the signal to be passed to a microcontroller.

[Download](#)[Favorite](#)

You will need five of the 10 kOhm resistors, both 1N4148 diodes, and a second TL072 chip. Warning... this will be the most difficult phase to assemble! Pay close attention to the pictures!

First, plug in a TL072 chip (chip C) and connect -9V rail to pin 4, the +9V rail to pin 8 and GND to pin 3, as shown in the first image.

Next, place a 10 kOhm resistor (let's call it resistor A) connecting pin 1 of the TL072 chip from the amplification phase and plug the other end into the row next to the 0.01uF capacitor's row. Use a jumper wire to connect this row to pin 2 of the second TL072 chip. The next 10 kOhm resistor we'll call resistor B. Resistor B's first pin should be plugged into the row where resistor A's second pin is plugged in and resistor B's other pin should be plugged into the row two down. Another 10 kOhm resistor's (resistor C) first pin should be plugged into the 16^{row 89} where resistor A's second pin terminated

(Same as resistor B) but the other part should be plugged into the next immediate row over. (See

advertisement

Download

Favorite

Now get out the two 1N4148 diodes. Diodes are polarized so be sure to pay attention what direction you plug them in! We'll call these diodes A and B. Plug diode A's positive end (end with black strip) into pin 1 of chip C and plug the negative end into the row of resistor C's second pin. Get diode B and plug the NEGATIVE end into pin 1 of chip c and plug the POSITIVE end into the row of resistor B's second pin. (See image #3)

Next, use two jumper wires to bridge the center gap for resistor C and B's rows. Use another jumper wire to connect the jumper wire's row connected to resistor B's row to pin 5 of chip C. Use another 10 kOhm resistor to connect the jumper wire's row connected to resistor C's row to pin 6 of chip C. Finally, use the last 10 kOhm resistor to connect chip C's pins 6 and 7. (See image #4).

Phew... that is for the rectifying phase! Next is the filter phase.

 Add Tip

 Ask Question

 Comment


Step 6: SIGNAL CONDITIONING -

advertisement

Download

Favorite

Smoothing + Amplification

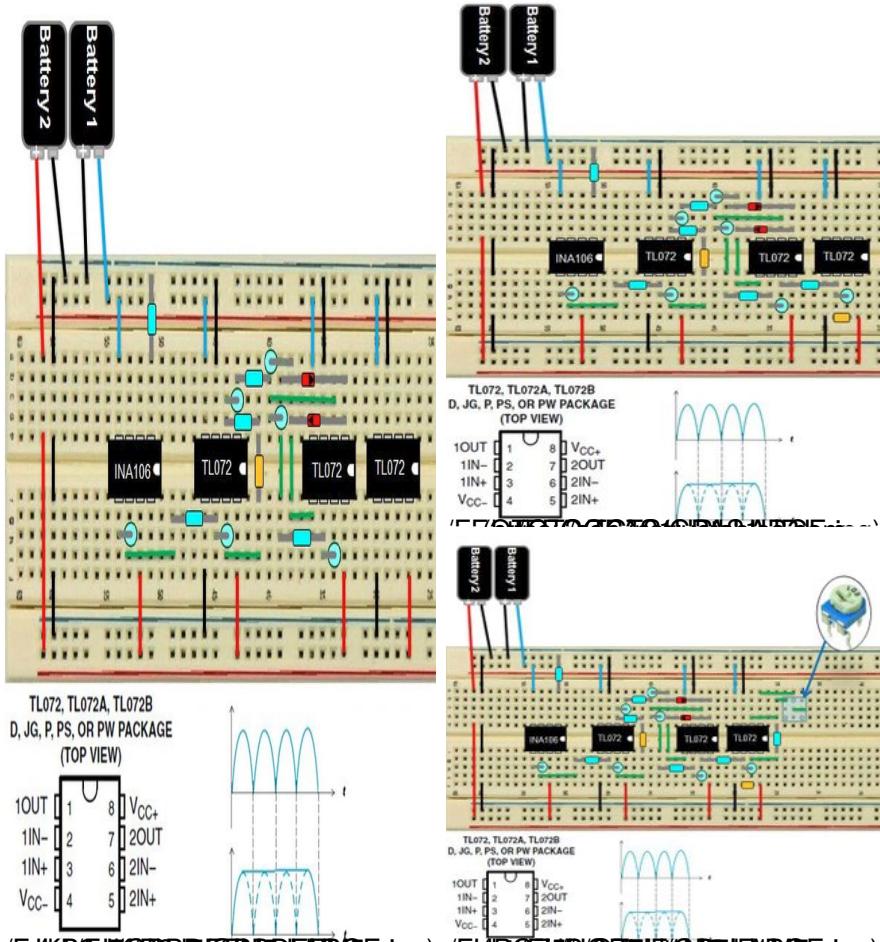

In this last phase of circuit assembly, we will be using an active low-pass filter to filter out the humps of our signal to produce a smooth signal for our microcontroller.

You will need the last TL072 chip (chip D), the two 80.8 kOhm resistors, the 100 kOhm trimmer, the 1 kOhm resistor and the 1.0 uF ceramic disc capacitor.

Now, grab one of the 80.6 kOhm resistors and connect one end to chip C's pin 7. Connect the other end to chip D's pin 6. Next grab the other 80.6 kOhm resistor use it to connect chip D's pin 6 and 7. Do the same thing for the 1.0 uF capacitor. (image #2)

That's the end of the filter circuit. However, since this is an active filter, there is a side effect of inverting the signal. We will need to invert the signal one more time (and have the ability to amplify it more if desired) using another inverting amplifier circuit with a trimmer configured as a variable resistor.

Use a jumper wire, connected to chip D's pin 7, and the 1 kOhm resistor to bridge the board's center gap. Use another jumper wire and connect the 1 kOhm resistor to chip D's pin 2. Next, place the trimmer one row over with the pins laid out and a jumper wire connecting two of the pins as pictured. Finally, place the last two jumper wires as indicated. (image #3)

By using a screw driver and turning the trimmer, you will be able to adjust the gain of your signal to account for different signal

Download

Favorite

advertisement


 Add Tip

 Ask Question

 Comment

Download

Step 7: Circuit Review

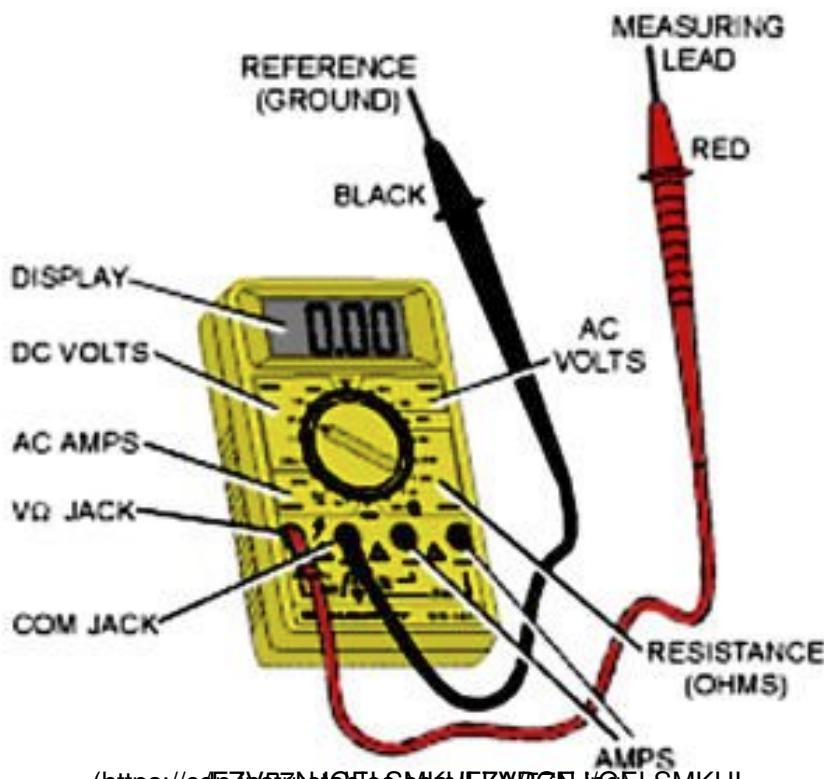

(Optional) If you have an oscilloscope and a wave generator handy, now would be a good time to step through the circuit and test each phase.

If you do not have an oscilloscope handy, go back and review your circuit connections step by step to make sure you have placed each

component correctly. Pay close attention to the power pins and connections of your chips. If


you have these incorrect, you could burn out

[Download](#)[Favorite](#)

your chips!

 [Add Tip](#) [Ask Question](#) [Comment](#)[Download](#)

Step 8: Electrode Cables

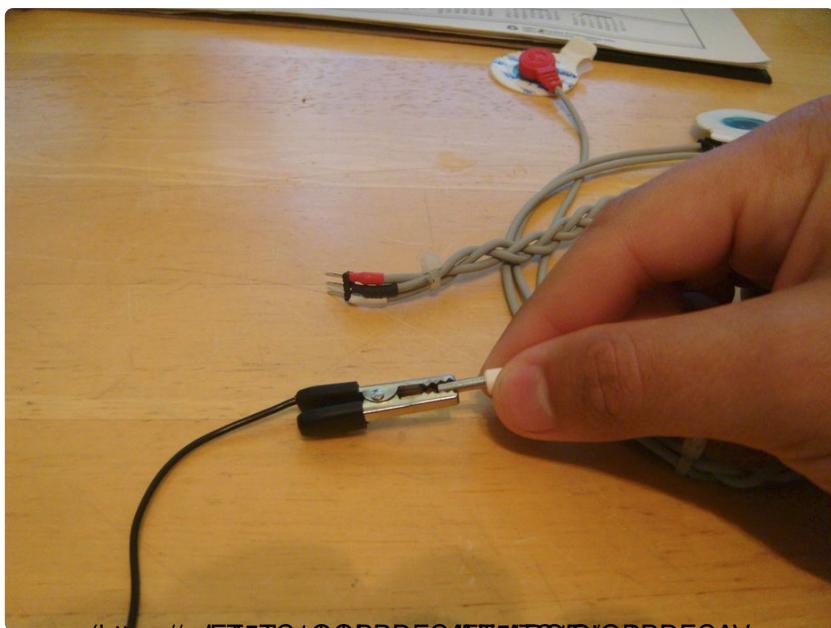

Next, you'll need to make some changes to the EMG electrode cables since I have been unable to find a vendor who sells the cable's style DIN connector's female compliment. (if any one has a suggestion please let me know!)

Grab a pair of scissors, wire cutters, wire strippers, pocket knife, etc.... basically anything

sharp and strip about a 1/4" of the end of the

7/16/18, 12:34 PM

advertisement

Download

Favorite

Next, clip an alligator cable to each of the wires. We will use these to connect the electrode cables to our breadboard with some jumper wire. You could do as I have done and strip the wire and then solder on terminal pins but it is not necessary and the alligator clips will do fine.

-💡 Add Tip

❓ Ask Question

💬 Comment

Download

Step 9: Surface Electrodes



For the electrode placement, you will need three surface electrodes.

want to target (for example I will be using my right bicep) and cleaning the skin thoroughly,

[Download](#)[Favorite](#)

place one electrode on your skin above the middle of the length of the desired muscle.

Let's call this the mid muscle electrode.

Next, place a second electrode at one end of the muscle. We'll call this the end muscle electrode.

Last, place the third electrode on a bony part of your body nearby the muscle group. We'll call this the reference electrode. For example, for the biceps, I am placing the reference electrode on the bony end of my forearm close to my elbow.

Using the snap connections of the electrode cables, snap each cable to each electrode.


Make a mental note of which color cable is attached to which electrode.

 [Add Tip](#) [Ask Question](#) [Comment](#)[Download](#)

Step 10: Connecting Electrode Cables

Download

Favorite

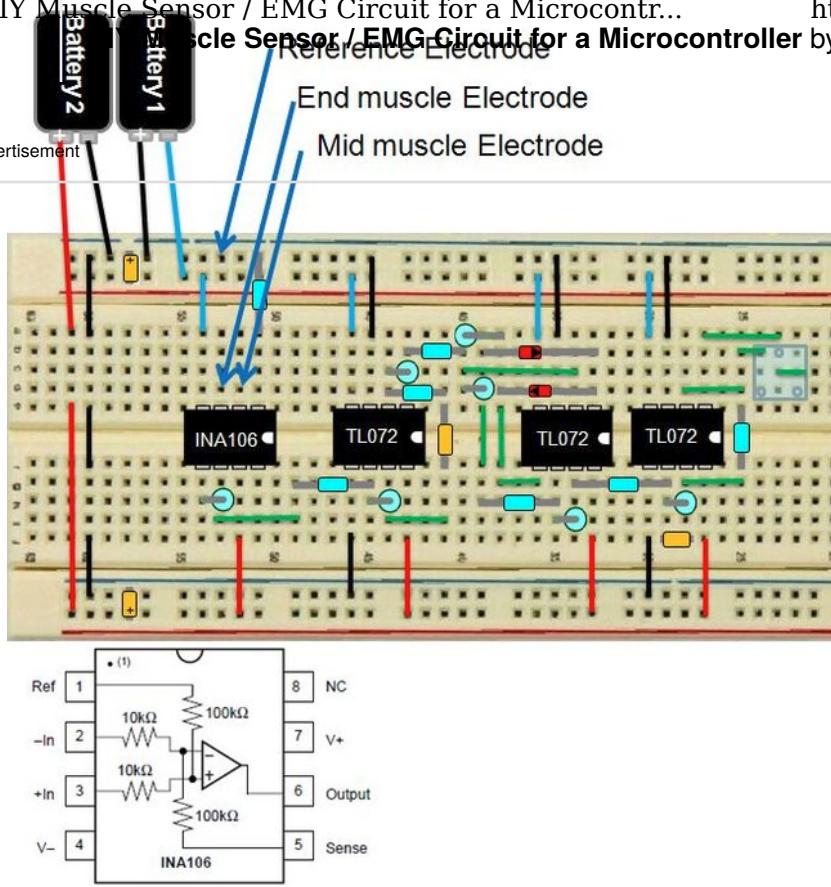

Now you are ready to connect your electrode cables to your circuit. Remember those pins on chip A that we put aside till later?

Connect the reference electrode to the GND rail of your circuit.

Connect the mid muscle electrode to chip A's pin 2

Connect the end electrode to chip A's pin 3

Lastly, we need to add some circuit protection via capacitors. Tantilium capacitors are polarized like the diodes we used earlier. These are easier to tell which is the positive pin and negative pin since one is always marked with a

GND rail, with the positive end connected to

the +9V rail. Connect the other 1.0 uF capacitor [Download](#)

[Favorite](#)

advertisment
to the -9V and GND rails, with the positive end
connected to the GND rail.

Now you'll ready to power on your circuit!


-💡- Add Tip

❓ Ask Question

💬 Comment

[Download](#)

Step 11: Connecting to a Microcontroller

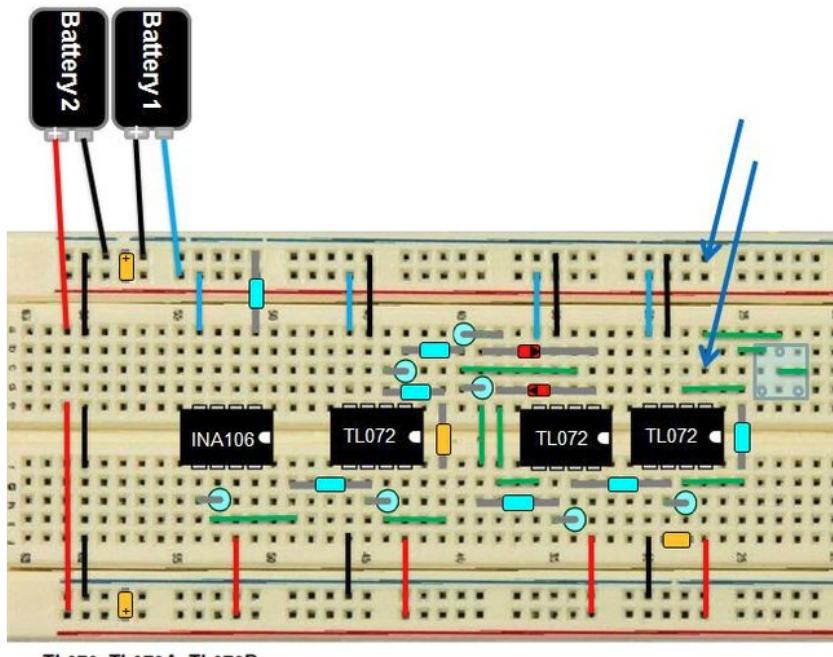

TL072, TL072A, TL072B
D, JG, P, PS, OR PW PACKAGE
(TOP VIEW)



DIX Muscle Sensor / EMG Circuit for a Microcontroller
DIY Muscle Sensor / EMG Circuit for a Microcontroller

<http://www.instructables.com/id/Muscle-EMG-Sen...>
by Advancer Technologies (/member/Advancer Technolog

circuit (by connecting the battery wire's we

disconnected earlier) and check the output

[Download](#)

[Favorite](#)

voltage with a multimeter to make sure it is within your microcontroller's analog input pin's tolerances. To do this, connect the negative multimeter probe to your GND rail and connect the positive probe to pin 1 of chip D. Make sure the voltage measured is less than the max voltage of your input pin!

If you've done that check and everything thing looks fine, use jumper wires to connect pin 1 of chip D to an analog input pin of your microcontroller and your GND rail to the GND pin of your microcontroller.

Congratulations you're done!

 Add Tip


 Ask Question

 Comment

[Download](#)

Step 12: Arduino Demo

advertisement

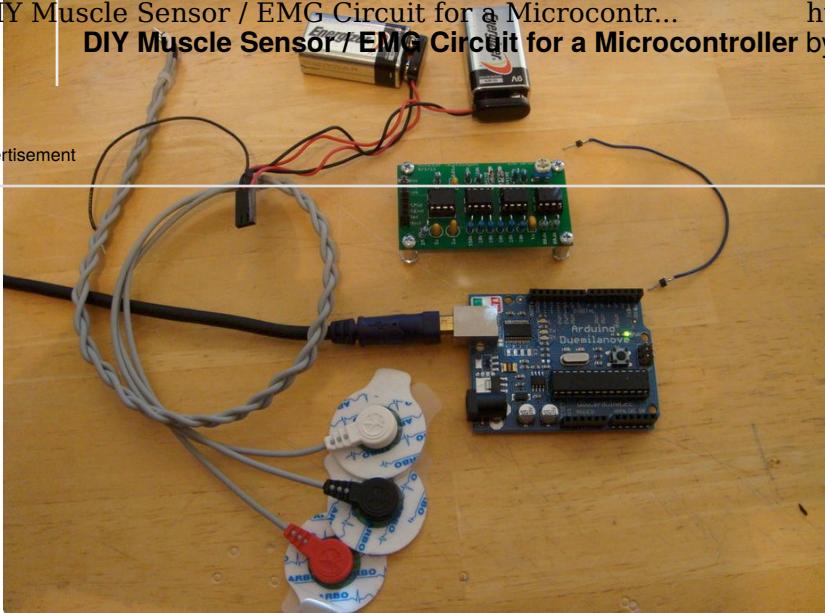[Download](#)[Favorite](#)


For this demo, we used an Arduino Duemilanove microcontroller hooked up to a PC running Processing visualization software.

Remember to visit us at
www.AdvancerTechnologies.com for kits and
fully assembled sensors!
([http://www.advancertechnologies.com
/p/muscle-sensors.html](http://www.advancertechnologies.com/p/muscle-sensors.html))

advertisement

[Download](#)[Favorite](#) [Add Tip](#) [Ask Question](#) [Comment](#)[Download](#)

Step 13: EMG Circuit Schematic

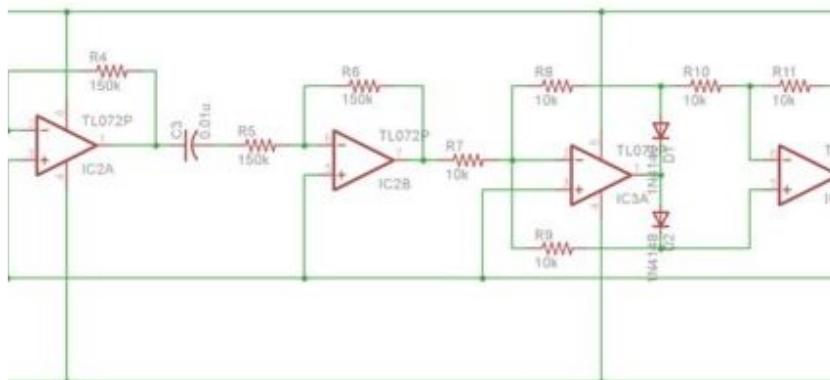

Advancer Techno
www.AdvancerTechnologies.com

DIV Muscle Sensor / EMG Circuit for a Microcontroller http://www.instructables.com/id/Muscle-EMG-Sen...
DIY Muscle Sensor / EMG Circuit for a Microcontroller by Advancer Technologies (/member/Advancer Technolog
[EMG schematic image](#)

advertisement (<http://www.advancertechnologies.com>

[Download](#)

[Favorite](#)

[/p/muscle-sensor-emg-circuit-kit-bronze.html](#) .

 Add Tip

 Ask Question

 Comment

[Download](#)

advertisement

advertisement

11 People Made This Project!

advertisement

[Download](#)[Favorite](#)

Trainer665 (/member
/Trainer665/) made it!

bobolgb (/member/bobolgb/)
made it!

SiddharthG16 (/member
/SiddharthG16/) made it!

Nour Abdel Latif Sanouree
(/member
/Nour+Abdel+Latif+Sanouree/)
made it!

OzoneAmanda (/member
/OzoneAmanda/) made it!

AhsanM18 (/member
/AhsanM18/) made it!

MarcoP142 (/member
/MarcoP142/) made it!

narendra1997 (/member
/narendra1997/) made it!

advertisement

[Download](#)[Favorite](#)[See 2 more that made it](#)

jerryliu (/member/jerryliu/)

made it!

Did you make this project? Share it with us!

[I Made It!](#)

Recommendations

[\(/id/Electronic-Cricket-Game/\)](/id/Electronic-Cricket-Game/)**Electronic Cricket Game** (/id/Electronic-Cricket-Game/)

by lonesoulsurfer (/member/lonesoulsurfer/) in Technology (/techn...

DIY Muscle Sensor / EMG Circuit for a Microcontr...

<http://www.instructables.com/id/Muscle-EMG-Sen...>

DIY Muscle Sensor / EMG Circuit for a Microcontroller by Advancer Technologies (/member/Advancer Technolog

advertisement

Download

Favorite



[\(/id/LED-DRAWING-PAD/\)](/id/LED-DRAWING-PAD/)

LED DRAWING PAD [\(/id/LED-DRAWING-PAD/\)](/id/LED-DRAWING-PAD/)

by Creativity Buzz (/member/Creativity%20Buzz/) in Leds (/techno...



[\(/id/Weather-Forecast-Clock-Using-Old-Alarm-and-Arduino/\)](/id/Weather-Forecast-Clock-Using-Old-Alarm-and-Arduino/)

Weather Forecast Clock Using Old Alarm and Arduino

[\(/id/Weather-Forecast-Clock-Using-Old-Alarm-and-Arduino/\)](/id/Weather-Forecast-Clock-Using-Old-Alarm-and-Arduino/)

by LenkaDesign (/member/LenkaDesign/) in Clocks (/technology/c...

DIY Muscle Sensor / EMG Circuit for a Microcontr...

<http://www.instructables.com/id/Muscle-EMG-Sen...>



advertisement



Download

Favorite

(/class/3D-CAM-and-CNC-Class/)



3D CAM and CNC Class (/id/3D-CAM-and-CNC-Class/)

689 Enrolled



(/contest/misuse/)



(/contest/oil/)



advertisement

[\(/contest/clocks2018/\)](/contest/clocks2018/)

[Download](#)

[Favorite](#)

CLOCKS — CONTEST —



[Add Tip](#)



[Ask Question](#)



[Post Comment](#)

We have a **be nice** policy.

Please be positive and constructive.

[Add Images](#)

[Post](#)

426 Discussions



FLIPPtronics (</member/FLIPPtronics>)
[\(/member/FLIPPtronics/\)](/member/FLIPPtronics/) /FLIPPtronics/

2 years ago

[Reply](#)

[Upvote](#)

How much do the materials for this cost in total? Is it cheaper than the pre-build myoware muscle sensors?



advertisement

(/member/Rom%C3%A1nV1/)

/member

/Rom%C3

Download

Favorite

%A1nV1/)

3 years ago

[Reply](#)[▲ Upvote](#)

what programs and code for arduino you used for the data acquisition and the visual representation of the emg signals?, thanks for your time and for your project (:

1 reply ▾



(/member/mosi0936/)

mosi0936 (/member

/mosi0936/)

7 days ago

[Reply](#)[▲ Upvote](#)

hi

im tring to make this circuit but i have question. could you tell me that which pins of this circuit should conect to arduinio? and if it is possible send me the picture of your arduino whent pins conected to it.

thanks

gmail: biopax.mirkazemi2016@gmail.com

(mailto:biopax.mirkazemi2016@gmail.com)



(/member/adityab98/)

adityab98 (/member

/adityab98/)

Question 24 days ago on

Introduction

[Answer](#)[▲ Upvote](#)

can you please suggest any replacement for INA106 because its not available here.



(/member/vaibhava31/)

vaibhava31 (/member

/vaibhava31/)

5 months ago

hello sir,

your work is really appreciating. i just want to know

[Download](#)

[Favorite](#)

what is use of 100 kohm trimmer

and can i use a regular 100k ohm resistor instead of
trimmer



(/member/shruikan27/)

shruikan27 (/member
/shruikan27/) 7 months ago

[Reply](#)

[▲ Upvote](#)

Where can we actually get the Processing
visualization software program used to test the
completed device? We have downloaded the Arduino
sample codes but when it comes to integrating it into
the processing software we are receiving certain
errors.

1 reply ▾



(/member/6_run/)

6_run (/member/6_run/)
Question 5 months ago on Step

13

[Answer](#)

[▲ Upvote](#)

Hi, how does one control 5 robotic fingers individually
using one muscle sensor.<http://sensor.how>
exactly does the sensor work with just 3 inputs.Won't
the other muscles interfere and change the value that
the sensor reads.



(/member/bakkkkkk/)

bakkkkkk (/member
/bakkkkkk/) 6 months ago

[Reply](#)

[▲ Upvote](#)

I am trying to observe the EMG raw data (output from
INA106), then the amplified data, rectified data and
36 of 31 the smoothed data, on an oscilloscope. Need help!
Can you or someone share the graph plots that are

7/16/18, 12:34 PM

advertisement

[Download](#)[Favorite](#)[\(/member/bakkkkkk/\)](/member/bakkkkkk/)

bakkkkkk (/member

/bakkkkkk/) 6 months ago

[Reply](#) [Upvote](#)

Can you please share the graphs plots obtained from each IC's outputs?

[\(/member/AhmedT125/\)](/member/AhmedT125/) /AhmedT125/

6 months ago

[Reply](#) [Upvote](#)

good

[\(/member/AhmedT125/\)](/member/AhmedT125/) /AhmedT125/

6 months ago

[Reply](#) [Upvote](#)

thanks

[\(/member/psuthar1/\)](/member/psuthar1/)

psuthar1 (/member

/psuthar1/) 7 months ago

[Reply](#) [Upvote](#)

which model of INO106 is used in this project. There are 5 different models are available on the site whose link you have given.

<http://www.ti.com/product/INA106/samplebuy>

[\(/member/shaon1333/\)](/member/shaon1333/)

shaon1333 (/member

/shaon1333/) 7 months ago

[Reply](#) [Upvote](#)

DIY Muscle Sensor / EMG Circuit for a Microcontroller... and <http://www.instructables.com/id/Muscle-EMG-Sen...>
DIY Muscle Sensor / EMG Circuit for a Microcontroller by Advancer Technologies (/member/Advancer Technolog what is the voltage and frequency range of this project?

Download

Favorite

advertisement



(/member/safsafg1/)

safsafg1 (/member

/safsafg1/) 8 months ago

Reply

▲ Upvote

What I would like to know about calculations, is how you set the values for C1 and C2

Thank you before



(/member/safsafgassim6/)

safsafgassim6

(/member

/safsafgassim6/)

8 months ago

Reply

▲ Upvote

What a benefit C1 and C2

More Comments

Post Comment

advertisement

Categories

Technology (/technology/)

Workshop (/workshop/)

Craft (/craft/)

Home (/home/)

Food (/food/)

Play (/play/)

Outside (/outside/)

Costumes (/costumes/)

About Us

Download We

Are

(/about/)

Why

Publish?

(/about

/create.jsp)

Jobs

(/community

/Positions-

available-

at-

Instructables/)

Contact

(/contact/)

Resources

Residency

Program

(<http://www.autodesk.com>)

/pier-9/residency

/home)

Community

(/topics/)

Sitemap

(/sitemap/)

Help (/id/how-to-

write-a-great-

instructable/)

Find Us

(<http://www.instagram.com/instructables/>)



(<http://www.pinterest.com/instructables/>)



(<http://www.facebook.com/instructables>)



(<http://www.twitter.com/instructables>)

© 2018 Autodesk, Inc.



AUTODESK. Make anything. (<http://www.autodesk.com>)

[Terms of Service](http://usa.autodesk.com/adsk/servlet/item?siteID=123112&id=21959721) |

[Privacy Statement](http://usa.autodesk.com/adsk/servlet/item?siteID=123112&id=21292079) | [Privacy settings](#)

[Legal Notices & Trademarks](http://usa.autodesk.com/legal-notices-trademarks/)